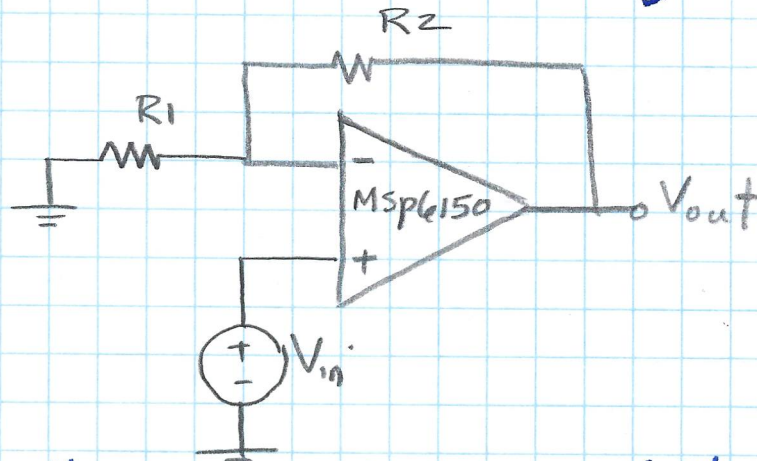


⇒ Noise Gain in op-Amp

Assume op-Amp is configured as non-inverting amplifier



If we apply Feedback Theory to above circuit we can write the following basic equations:

$$A_{cl} = \frac{A}{1 + A\beta} \quad \begin{array}{l} A_{cl} = \text{closed-loop Gain} \\ A = \text{open-loop Gain} \end{array} \quad \beta = \frac{R_1}{R_1 + R_2}$$

β ⇒ is the feedback factor that shows the portion of feedback signal to the input

$$A_{cl} = \frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta} = \frac{1}{\beta} \frac{1}{\frac{1}{A\beta} + 1} \quad \text{if } \frac{1}{A\beta} \ll 1 \text{ Then}$$

$$A_{cl} = \frac{1}{\beta} \left[1 - \frac{1}{A\beta} \right] \quad \text{if } A \Rightarrow \infty \text{ then } A_{cl} \approx \frac{1}{\beta} \text{ ideal}$$

$\frac{1}{\beta}$ is called Noise Gain

$$\% \text{ Gain Error} = \frac{\frac{1}{\beta} - \frac{1}{\beta} \left[1 - \frac{1}{A\beta} \right]}{\frac{1}{\beta}} \times 100$$

$$\% \text{ Gain Error} = \frac{100}{A\beta}$$

Monolithic Silicon Power


F. Moraveji

Application Note 2 (OP-Amps)

3/8/2021

⇒ Assume op-amp has Single Pole roll off
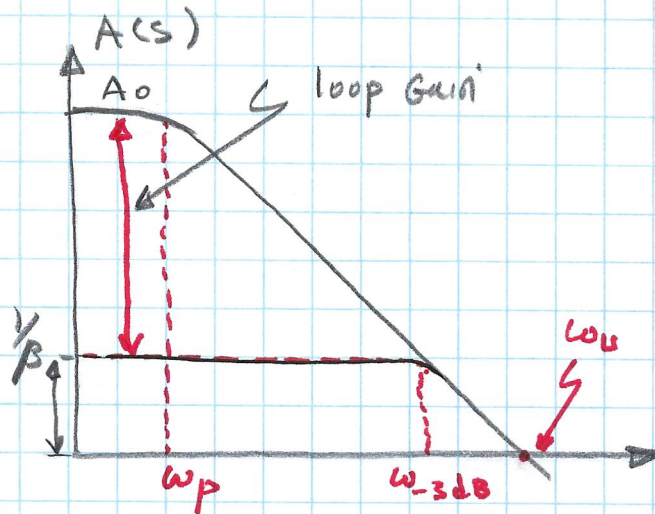
$$A(s) = \frac{A_0}{1 + j\omega/\omega_p}$$



$$A_{cl} = \frac{A(s)}{1 + \beta A(s)} \Rightarrow A_{cl} = \frac{A_0}{1 + A_0\beta + j\omega/\omega_p}$$

$$A_{cl} = \frac{A_0}{1 + A_0\beta} \cdot \frac{1}{\left[1 + j\frac{\omega}{\omega_p(1 + A_0\beta)}\right]} \quad \text{and if } A_0\beta \gg 1$$

$$A_{cl} = \frac{1}{\beta} \frac{1}{1 + j\frac{\omega}{\omega_u\beta}} = \frac{1}{\beta} \frac{1}{1 + j\frac{\omega}{\omega_{-3dB}}}$$

$$\omega_{-3dB} = \frac{\omega_u}{1/\beta} \quad 1/\beta = \text{Noise Gain} = \text{closed-loop Gain}$$

$$\omega_u = \text{OP-Amp Unity Gain Frequency} = A_0\omega_p$$

$$\text{Therefore: } \omega_{-3dB} = \frac{\omega_u}{\text{Closed-loop Gain}}$$