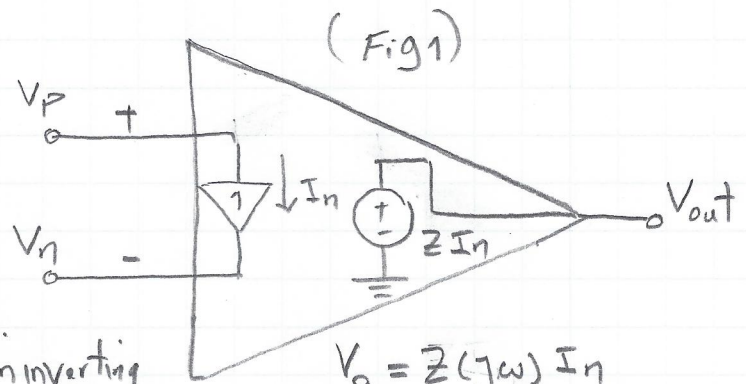


### ⇒ Current Feedback Amplifier Analysis

- In Current Feedback Amplifiers, Forward gain is Transimpedance  $Z(j\omega)$
- The input voltage  $V_i$  is imposed on inverting input via 1x Buffer
- The closed-loop bandwidth does not depend on closed-loop gain!
- Feedback node is low-impedance and Feedback quantity is current



⇒  $V_i$  is imposed on noninverting node via 1x buffer

$$V_o = Z(j\omega) I_n$$

⇒ By applying Superposition


$Z(j\omega) = \text{Transimpedance Gain}$

$$I_n = \frac{V_i}{R_1 + R_2} - \frac{V_o}{R_2}$$

( $V_{out}=0$ ) ( $V_i=0$ )

$$V_o = I_n Z(j\omega)$$
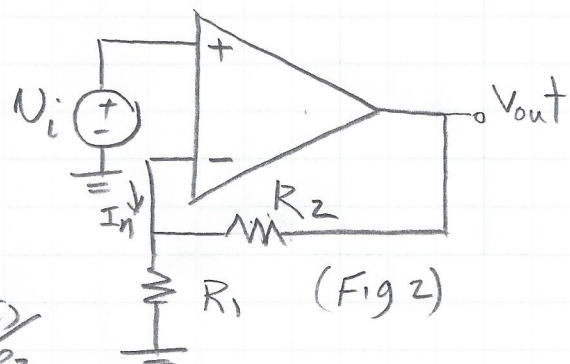
$$\frac{V_o}{V_i} = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{R_2} \frac{Z(j\omega)}{1 + \frac{Z(j\omega)}{R_2}}$$



$$1 + \frac{R_2}{R_1} = \text{closed-loop Gain}$$

$$\frac{Z(j\omega)}{R_2} = \text{Loop Gain}$$

# Monolithic Silicon Power

F. Moraveji

## OP-Amp White Paper 1 CFA

3/12/2021

For the current-feedback amplifier depicted in Fig 2 the closed-loop gain can be written as

$$\frac{V_o}{V_i} = \left(1 + \frac{R_z}{R_1}\right) \frac{1}{R_z} \frac{Z(j\omega)}{1 + \frac{Z(j\omega)}{R_z}} \quad \text{where } \frac{Z(j\omega)}{R_z} = \text{loop-gain}$$

The closed-loop transimpedance gain is equal to

$$\frac{V_o}{I_i} = \frac{Z}{1 + ZY} = Z_f(j\omega) \quad \text{if } ZY \gg 1 \quad Z_f(j\omega) = \frac{1}{Y}$$


$$Z(j\omega) = \text{open-loop Transimpedance Gain} = \frac{Z_o}{1 + j f/f_a}$$

$$\frac{V_o}{V_i}(j\omega) = \left(1 + \frac{R_z}{R_1}\right) \frac{1}{R_z} \frac{Z(j\omega)}{1 + \frac{Z(j\omega)}{R_z}}$$

$$\text{For } f \gg f_a \quad Z(j\omega) = \frac{Z_o f_a}{j f}$$

$$\frac{V_o}{V_i}(j\omega) = \left(1 + \frac{R_z}{R_1}\right) \frac{\frac{Z_o f_a}{j f}}{R_z + \frac{Z_o f_a}{j f}}$$
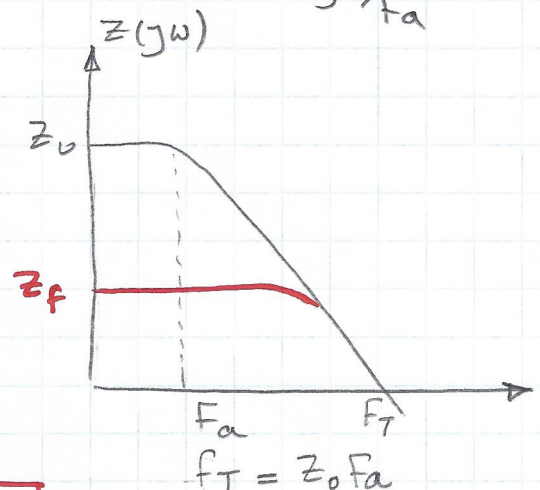
$$\frac{V_o}{V_i}(j\omega) = \left(1 + \frac{R_z}{R_1}\right) \frac{1}{1 + j \frac{f}{f_A}}$$



$$f_T = Z_o f_a$$

$$f_A = \frac{f_T}{R_z}$$

where  $f_A = \frac{Z_o f_a}{R_z} \Rightarrow$  As it can be seen, the closed

loop bandwidth of current-feedback amplifier is independent of noise gain  $1 + \frac{R_z}{R_1}$ . It is inversely

proportional to  $R_z$  (feedback resistor) and directly proportional to corner frequency  $f_a$  of transimpedance


# Monolithic Silicon Power

F. Moraveji


Op-Amp White Paper 1 CFA

3/12/2021

⇒ Basic Current Feedback Topology

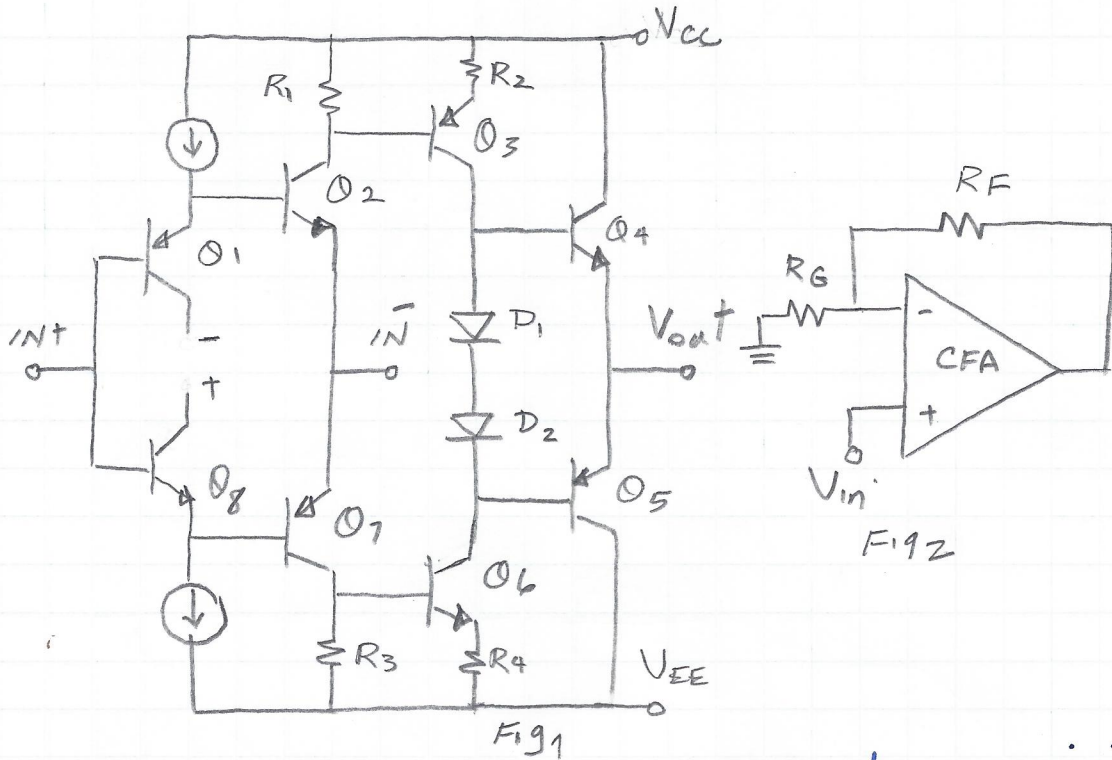


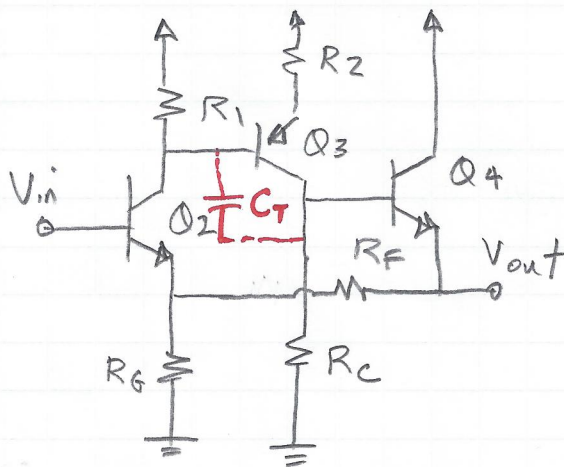⇒ In order to analyze above circuit, a simplified half circuit can be used



Series-shunt Feedback

Fig 3

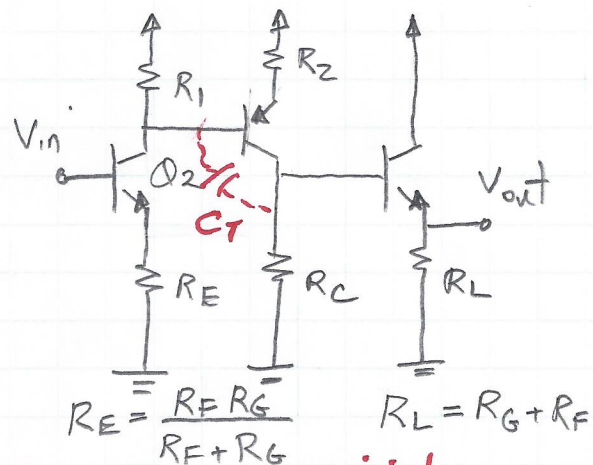

Open-loop circuit

Fig 4

$$R_E = \frac{R_F R_G}{R_F + R_G}$$

$$R_L = R_G + R_F$$

# Monolithic Silicon Power

F. Moraveji

OP-Amp white Paper 1 CFA

3/12/2021

⇒ Half Circuits of Fig<sub>3</sub> and Fig<sub>4</sub> Can be used to better understand Current Feedback Amplifiers

Fig<sub>4</sub> is the open-loop circuit for Fig<sub>3</sub> which takes into account the loading effect of feedback resistors  $R_F$  &  $R_G$


From Fig<sub>4</sub>, the open-loop DC gain is:

$$A_{DC} = \frac{R_1}{R_E} \cdot \frac{R_C}{R_2} \quad \omega_p = \frac{1}{R_1 \left( \frac{R_C}{R_2} C_T \right)}$$

← Miller effect →

Now define Transresistance  $Z_T = \frac{R_1 R_C}{R_2}$  then we

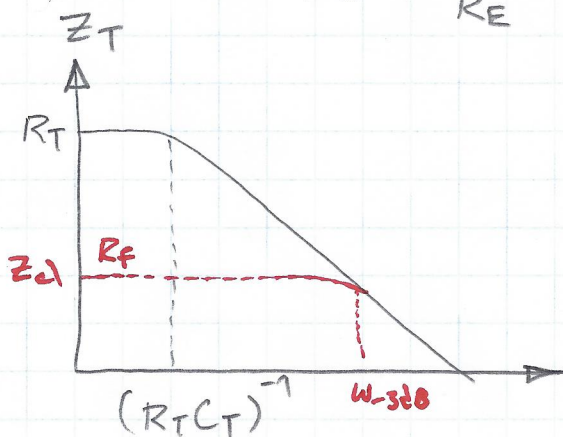can write  $A_{DC} = \frac{Z_T}{R_E}$   $\omega_p = \frac{1}{R_T C_T}$



$$A(j\omega) = \frac{R_T}{R_E} \frac{1}{1 + j\omega/\omega_p} = \frac{R_T}{R_E} \frac{1}{1 + j\omega R_T C_T} = \frac{V_o}{V_{in}}$$

$$\frac{V_o}{V_{in}} \cdot R_E = \frac{R_T}{1 + j\omega R_T C_T} \Rightarrow I_{in} = \frac{V_{in}}{R_E}$$

$$\frac{V_o}{I_{in}} = Z_T(j\omega) = \frac{R_T}{1 + j\omega R_T C_T} \quad \text{Eq. 1}$$

⇒ How To Calculate closed-loop Transimpedance in Current-Feedback Amplifiers

In order to find the closed-loop Transimpedance  $Z_{cl}(j\omega)$  which is set by resistors  $R_F$  &  $R_G$  in Fig. 3, we can use the general closed-loop equation for series-shunt feedback

$$Z_{cl} = \frac{V_o}{I_i} = \frac{Z_T(j\omega)}{1 + Z_T(j\omega)Y(j\omega)} \quad \text{Eq. 2}$$

$$Z_T(j\omega) = \frac{R_T}{1 + j\omega R_T C_T} \quad \& \quad Y(j\omega) = R_F$$

After substituting for  $Z_T(j\omega)$  &  $Y(j\omega)$  in Eq. 2 and assuming  $\frac{R_T}{R_F} \gg 1$

$$Z_{cl}(j\omega) = \frac{R_F}{1 + j\omega R_F C_T}$$

$$\omega_{-3dB} = \frac{1}{R_F C_T}$$

⇒ It can be seen from these two key equations that in current-feedback amplifiers, the closed-loop -3dB bandwidth is set by feedback resistor  $R_F$  and total internal capacitor  $C_T$